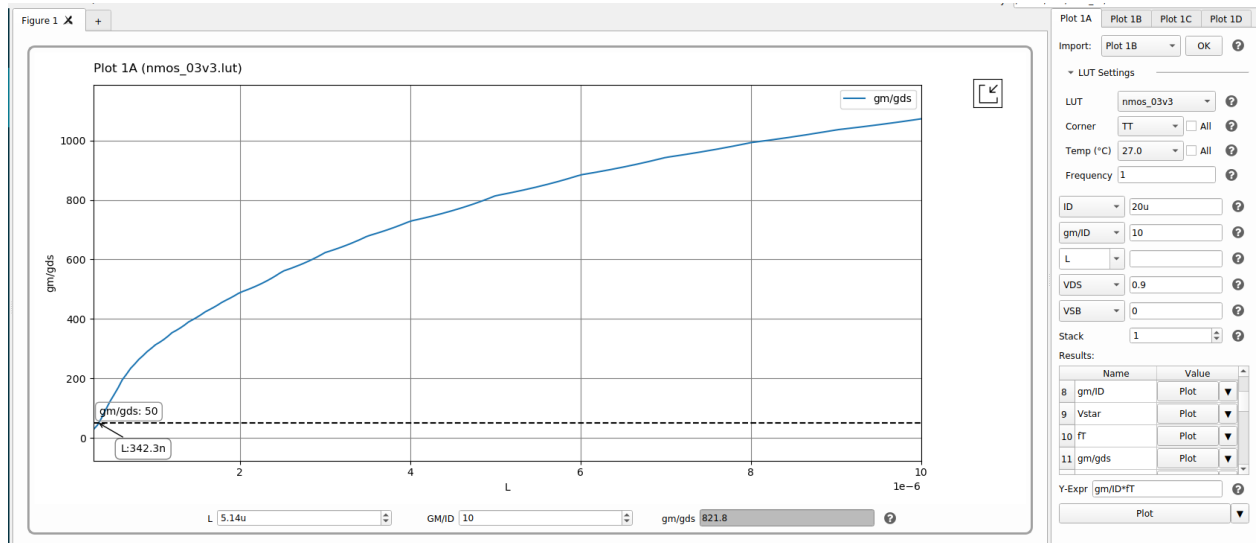


Lab 03


PART 1: Sizing chart:

- **Analysis:**


- We need to get $\frac{gm}{ID} = 10$ and $ID = 20 \mu A$. First, we will choose L.



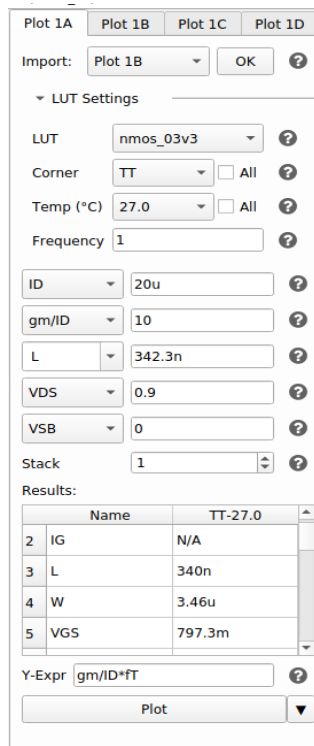
- Getting important parameters like W and VGS we get $W = 3.46 \mu m$.



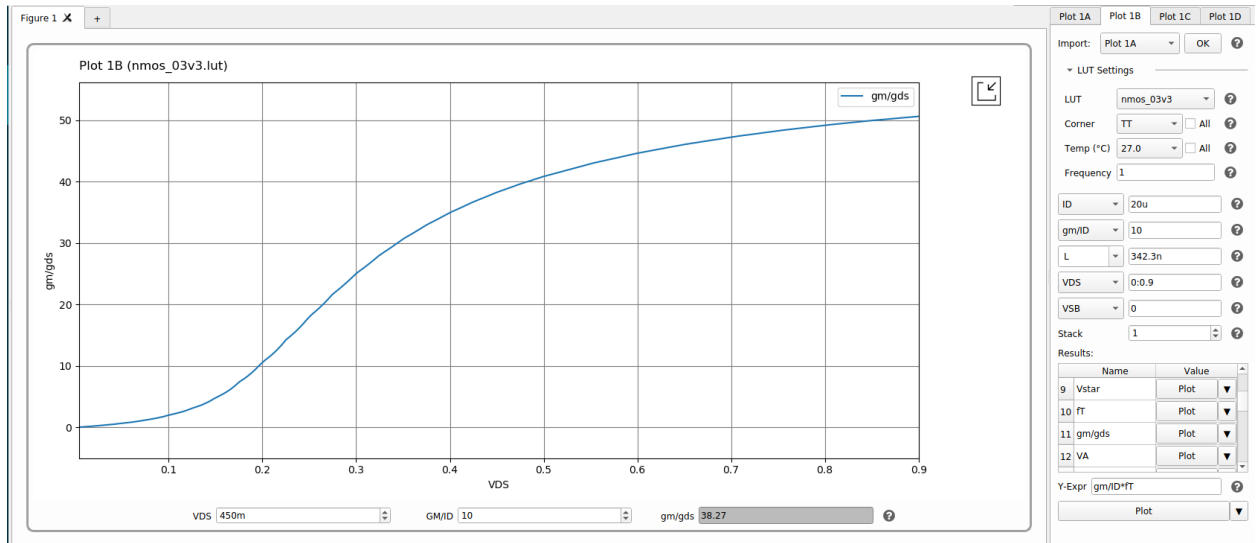- Notice that gm/gds depends on V_{DS} the graph for $L=342nm$.



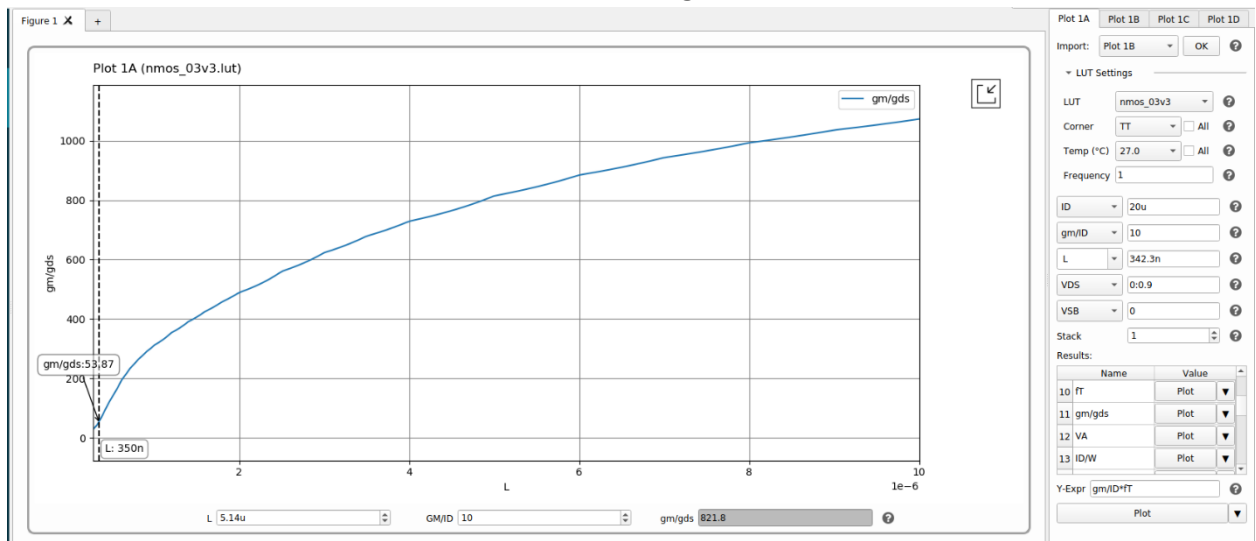- We will choose $L=350nm$ to guarantee the specs on $gm * r_o \geq 50$.



- Getting W for $L=350nm$ we get $W \approx 3.5 \mu m$

Parameters:

- ID: 20u
- gm/ID: 10
- L: 350n
- VDS: 0.9
- VSB: 0
- Stack: 1


Results:

Name	TT-27.0
1 ID	20u
2 IG	N/A
3 L	350n
4 W	3.49u

Y-Expr: $gm/ID*IT$

Plot


- For the cascode amplifier when we use the same sizing VDS will be 0.45v then
 $\frac{gm}{gds} = 41.65$.

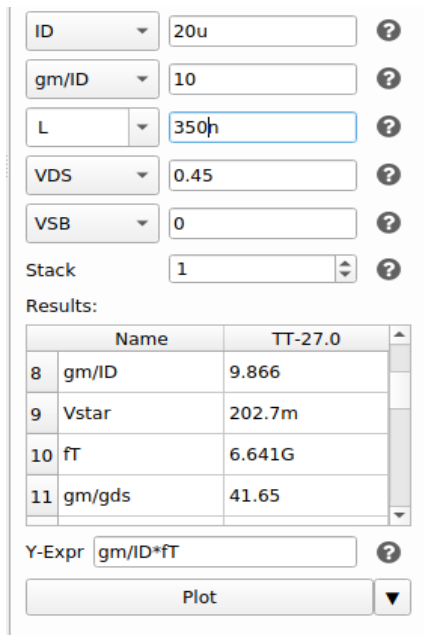

PART 2: Cascode for Gain:

1. OP Analysis:

- Schematic with DC OP Annotation:

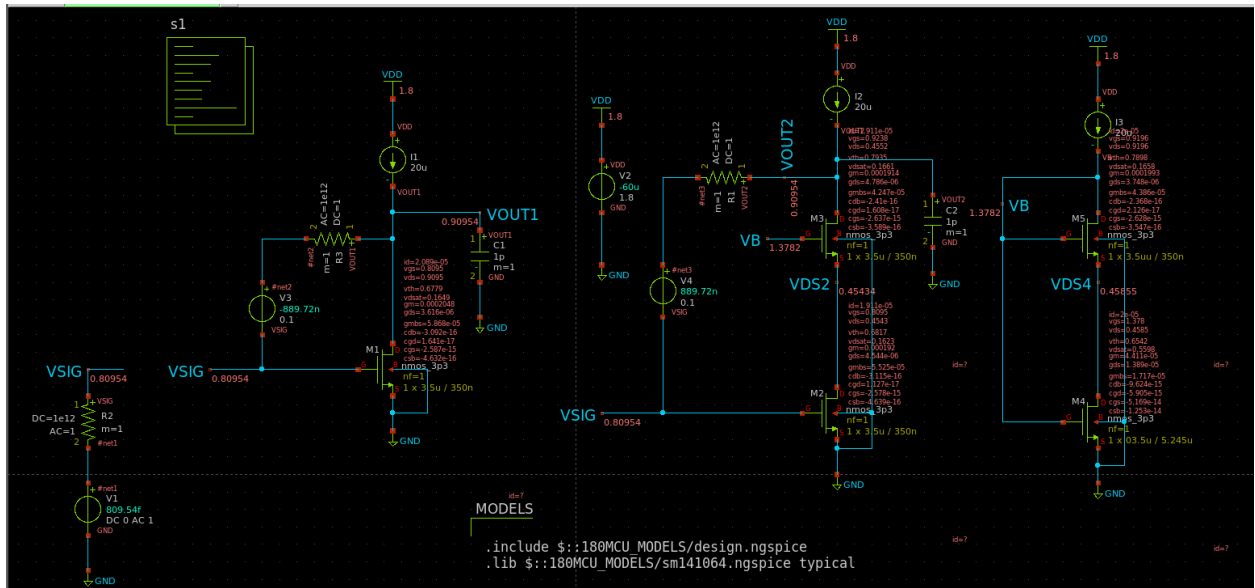

- **Choosing VB:**

- We find that the value of $VB = VGS3 + VDS2$. First, we will get $VGS3$ from sizing assistant. We found that $VGS3 = 927.7\text{mV}$.

Plot 1A Plot 1B Plot 1C Plot 1D

Import: Plot 1B OK ?

LUT Settings

LUT: nmos_03v3 ?

Corner: TT ? All ?

Temp (°C): 27.0 ? All ?

Frequency: 1 ?

ID: 20u ?

W: 3.5u ?

L: 350n ?

VDS: 0.45 ?

VSB: 0.45 ?

Stack: 1 ?


Results:

Name	TT-27.0
3 L	350n
4 W	3.5u
5 VGS	927.7m
6 VDS	450m

Y-Expr: gm/ID*FT ?

Plot

- We will assume $VDS2 \approx 0.45\text{V}$ then $VB = 1.377\text{V}$.
- Now to get the value of $V3$ and $V4$ dc voltages on the schematic above we know that $VDS = 0.9\text{V}$ and we got VGS in the first part approximately 0.8V then $V3 = V4 = 0.1\text{V}$.
- We will use the value of VB we got to calculate the length of the lower device (M4) of the magic battery. We have the width is constant. We get $L = 5.245\mu\text{m}$.

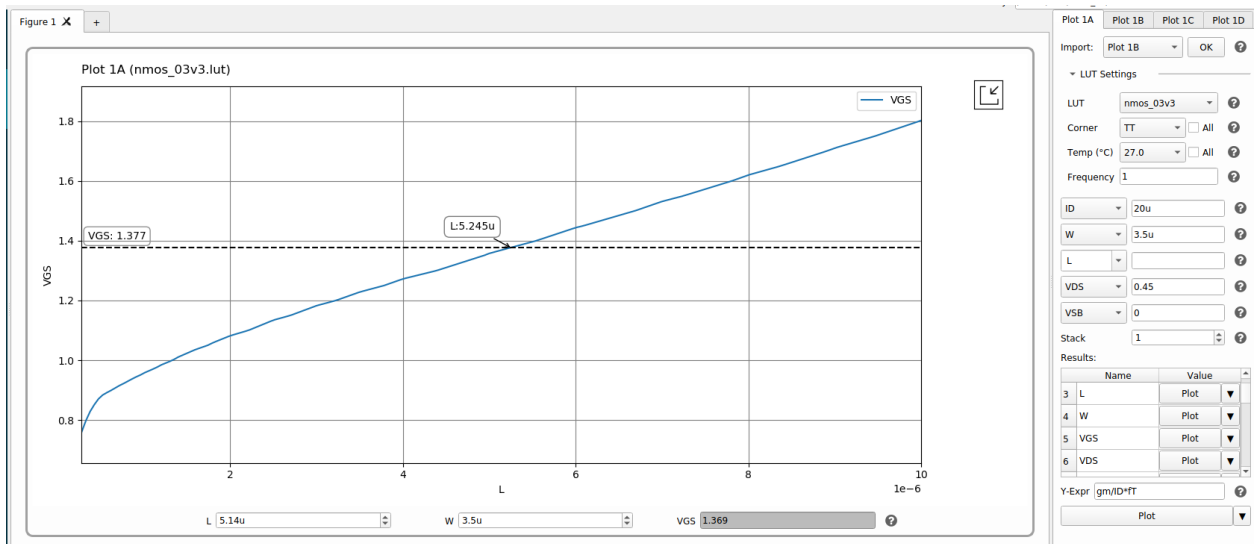


- Note: the DC OP annotations are on the schematic in p.3.
- Check that all transistors operate in saturation:
All transistors are in saturation except M4 as $V_{DS4}=0.4585\text{v} < V_{DSsat4}=0.5598\text{v}$ but for the rest of transistors $V_{DS} > V_{DSsat}$ so they are in saturation.
- Not all the transistors have the same V_{th} . The transistors (M1,M2,M4) almost have the same V_{th} and (M3,M5) almost have the same V_{th} . M3 and M5 have higher V_{th} as they suffer from bulk effect which increases the V_{th} .
- $gm > g_{ds}$
- $gm > g_{mb}$
- $cgs > cgd$
- $csb > cdb$
- For the (M4) which is in triode ($gm > g_{ds}$, $gm > g_{mb}$, $cgs > cgd$, $csb > cdb$)

2. AC Analysis:

- calculate parameters (DC gain, BW, GBW, and UGF) and export them to a text file:

```
1 max_gain_cs = 5.663693e+01
2 bw_cs = 5.755274e+05
3 gbw_cs = 3.259611e+07
4 ugf_cs = 3.267548e+07
5 max_gain_casc = 2.107317e+03
6 bw_casc = 1.423088e+04
7 gbw_casc = 2.998898e+07
8 ugf_casc = 3.015883e+07
```

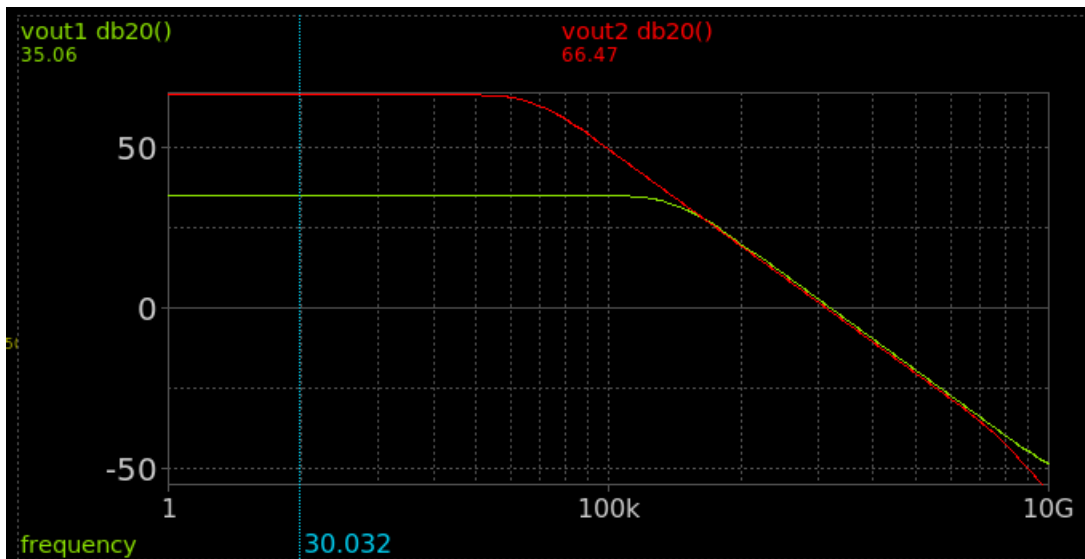- Bode plot (magnitude) of CS and cascode in dB:



- **Hand Analysis:**

- DC gain: for CS $|A| = \frac{gm}{g_{ds}} = 56.6$, and in dB it will be 35.06 dB.
For cascode $|GM| = gm1 = 192\mu S$
 $R_{out} = r_{o2} + r_{o1} + (gm2 + g_{mb2})r_{o1}r_{o2} = 11.158M\Omega$
 $|A| = 2142$, and in dB will be 66.6 dB.
- Calculating BW we can neglect other capacitances at output node as they are a lot less than CL. The output node is dominant so we will only consider it.
for CS $BW = \frac{1}{2\pi * r_{o1} * C_L} = 575.5KHz$
For cascode $BW = \frac{1}{2\pi * R_{out} * C_L} = 14.26KHz$
- GBW: for CS $GBW = A * BW = 32.57 MHz$
For cascode $GBW = A * BW = 30.54MHz$
- UGF: for first order systems $UGF \approx GBW$ and for CS and cascode we can consider them first order as we have a dominant pole.

- **Common Source Results comparison:**

	Analytical	simulation
DC gain	56.6	56.6
BW	575.5KHz	575.5KHz
GBW	32.57MHz	32.596MHz
UGF	32.57MHz	32.67MHz

- **Cascode Results comparison:**

	Analytical	simulation
DC gain	2142	2107
BW	14.26KHz	14.23KHz
GBW	30.54MHz	29.98MHz
UGF	30.54MHz	30.16MHz


- **Comment on results:**

The cascode for gain topology gives higher gain than the common source due to increasing the R_{out} but it decreases the BW (the range of frequency it works properly at) and the GBW which is a measure for speed stays almost constant as the output node is dominant.

PART 3: Cascode for BW:

1. OP Analysis:

- **Schematic and DC OP annotation:**

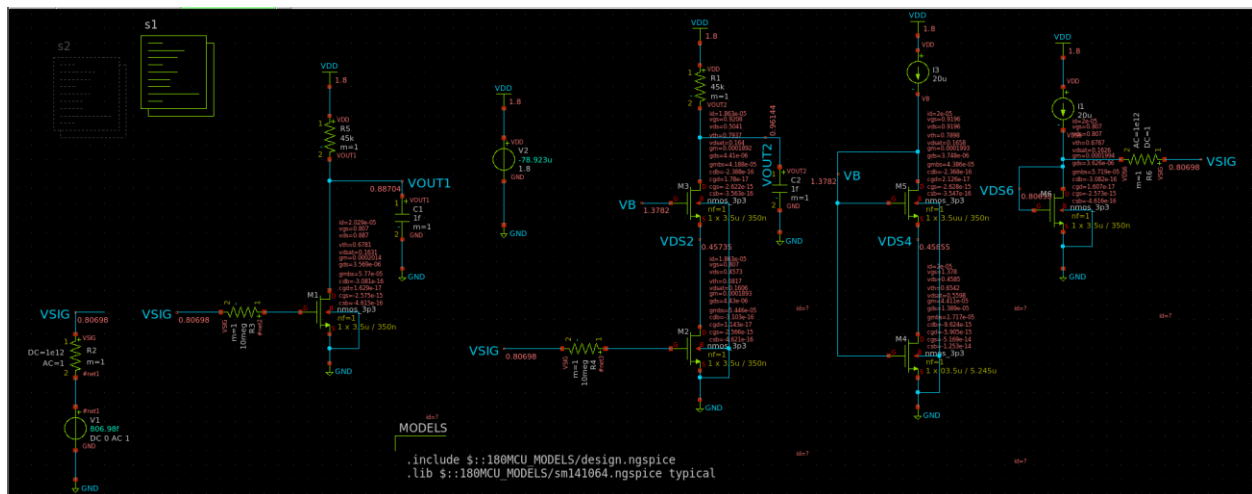


- Calculating R_D : We know that $I_D \approx 20\mu A$ as we use replica biasing by M6. If we want $V_{DS}=0.9$ then $R_D = \frac{0.9}{20 \times 10^{-6}} = 45k\Omega$.
- All transistors are in saturation except M4 as ($V_{DS4}=0.4585$) < ($V_{DSsat}=0.5598V$).

2. AC Analysis:

- calculate parameters (DC gain, BW, GBW, and UGF) and export them to a text file:

```
1 max_gain_cs = 7.806966e+00
2 bw_cs = 1.695066e+06
3 gbw_cs = 1.323332e+07
4 ugf_cs = 1.318210e+07
5 max_gain_casc = 8.331485e+00
6 bw_casc = 3.008329e+06
7 gbw_casc = 2.506385e+07
8 ugf_casc = 2.486351e+07
```

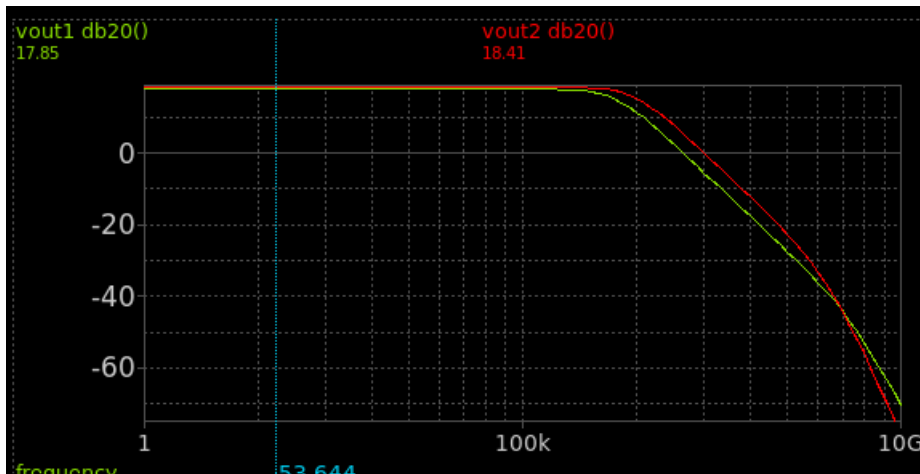- Bode plot (magnitude) of CS and cascode in dB:



- We will use the capacitors from ADT values for as xschem values aren't accurate.
For CS (M1) → $C_{GS}=3.239 \text{ fF}$, $C_{GD}=605.2 \text{ aF}$.
For cascode (M2) → $C_{GS}=3.255 \text{ fF}$, $C_{GD}=675 \text{ aF}$.
- DC gain: for CS $|A| = gm(RD//ro) = 7.82$, and in dB it will be 17.87 dB.
For cascode $|GM| = gm1 = 192 \mu S$
 $R_{out}' = ro2 + ro1 + (gm2 + gmb2)ro1ro2 = 11.158 M\Omega$
 $R_{out} = RD//R_{out}' = 44.82 K\Omega$
 $|A| = 8.6$, and in dB will be 18.69 dB
- Calculating BW we know that input node is dominant.
for CS $BW = \frac{1}{2\pi * R_{sig} * (C_{gs} + (1+A) * C_{gd})} = 1.855 \text{ MHz}$
For cascode $BW = \frac{1}{2\pi * R_{sig} * (C_{gs} + 2 * C_{gd})} = 3.577 \text{ MHz}$
- GBW: for CS $GBW = A * BW = 14.5 \text{ MHz}$
For cascode $GBW = A * BW = 30.76 \text{ MHz}$
- UGF: for first order systems $UGF \approx GBW$ and for CS and cascode we can consider them first order as we have a dominant pole.

- Common Source Results comparison:

	Analytical	simulation
DC gain	7.82	7.8
BW	1.855MHz	1.695MHz
GBW	14.5MHz	13.23MHz
UGF	14.5MHz	13.18MHz

- **Cascode Results comparison:**

	Analytical	simulation
DC gain	8.6	8.33
BW	<i>3.577MHZ</i>	<i>3.008MHz</i>
GBW	<i>30.76MHz</i>	<i>25.06MHz</i>
UGF	<i>30.76MHz</i>	<i>24.86MHz</i>

- Note that the results a bit off the capacitor values may be the problem.
- Comment on results:
Cascode for BW gives almost the same gain (a little higher) and higher BW so it gives higher GBW than the normal common source.