


Lab 06

Part 1: Differential Amplifier Design:

- Specs:

Parameter	value
VDD	1.8V
ISS	40 μ A
Differential gain	8
CM output level	0.6
Load capacitance	1pF

- Schematic:

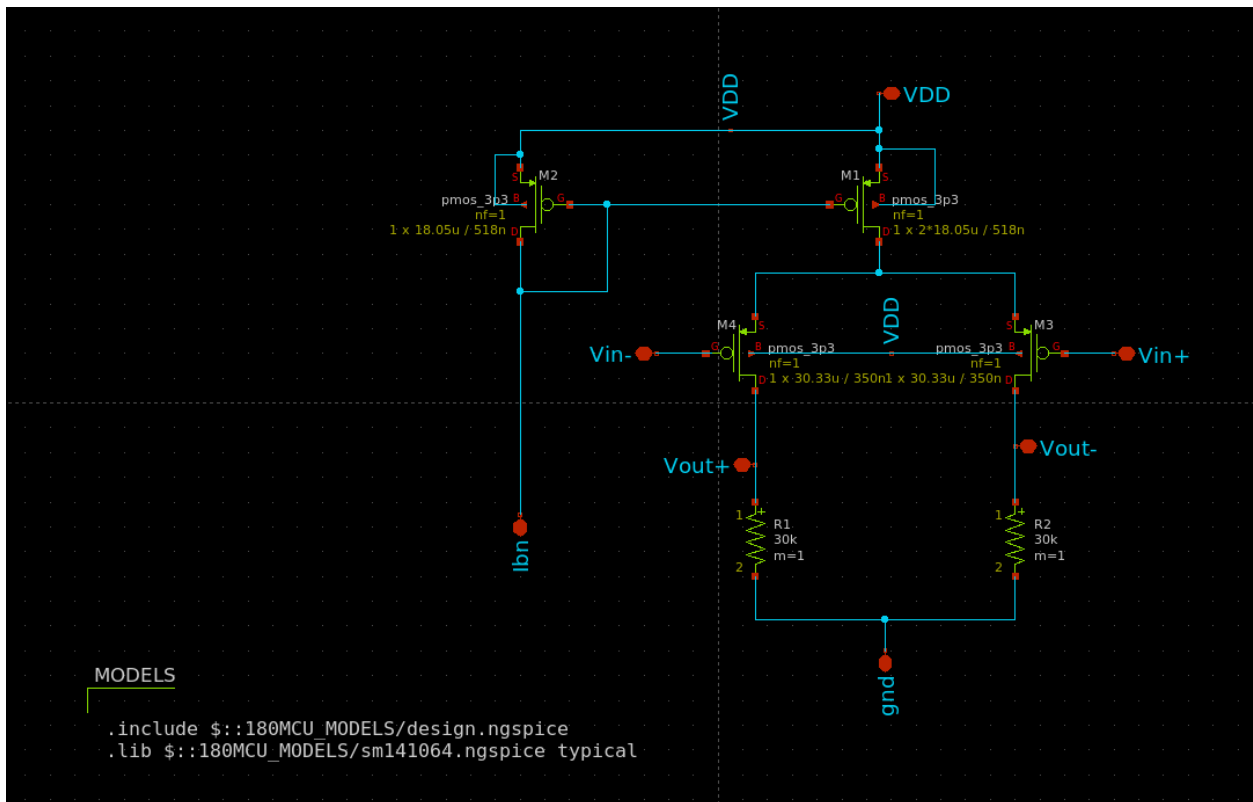

- Choose **RD** to meet the CM output level spec:

Each branch will have $20\mu A$ then $0.6 = 20\mu A * RD$ then $RD = 30K\Omega$.

- Choose **V*** to meet the differential gain spec:

$$V^* = \frac{1.82 * V_{RD}}{A_v} = \frac{1.82 * 0.6}{8} = 136.5mV.$$

- Assume we will set **VDS** of the tail current source to **300mV** to allow more output swing.

Report the input pair sizing using SA:

Plot 1A Plot 1B Plot 1C Plot 1D

Import: Plot 1B OK ?

LUT Settings

LUT: pmos_03v3 ?

Corner: TT ? All ?

Temp (°C): 27.0 ? All ?

Frequency: 1 ?

ID: 20u ?

Vstar: 136.5m ?

ro: 300k ?

VDS: 0.9 ?

VSB: 0.3 ?

Stack: 1 ?

Results:

Name	TT-27.0
1 ID	20u
2 IG	N/A
3 L	350n
4 W	30.33u

Y-Expr: gm/ID*ft ?

Plot

Plot 1A Plot 1B Plot 1C Plot 1D

Import: Plot 1B OK ?

LUT Settings

LUT: pmos_03v3 ?

Corner: TT ? All ?

Temp (°C): 27.0 ? All ?

Frequency: 1 ?

ID: 20u ?

Vstar: 136.5m ?

ro: 300k ?

VDS: 0.9 ?

VSB: 0.3 ?

Stack: 1 ?

Results:

Name	TT-27.0
5 VGS	940.4m
6 VDS	900m
7 VSB	300m
8 gm/ID	14.28

Y-Expr: gm/ID*ft ?

Plot

Plot 1A Plot 1B Plot 1C Plot 1D

Import: Plot 1B OK ?

LUT Settings

LUT: pmos_03v3 ?

Corner: TT ? All ?

Temp (°C): 27.0 ? All ?

Frequency: 1 ?

ID: 20u ?

Vstar: 136.5m ?

ro: 300k ?

VDS: 0.9 ?

VSB: 0.3 ?

Stack: 1 ?

Results:

Name	TT-27.0
22 VDSAT	122m
23 cgg	41.16f
24 cdd	17.87f
25 csg	20.29f

Y-Expr: gm/ID*ft ?

Plot

We got sizing of the input pair: $\frac{W}{L} = \frac{30.33\mu m}{350nm}$ and we got VGS and VDSsat as we will need them I hand analysis.


- Given the above assumption for **VDS** of the tail current source, calculate the required CM input level:

$$V_{CM} = -|V_{GS4}| + 1.5 = -0.94 + 1.5 = 560mV$$


- **Tail current source sizing:**

- **Given the compliance voltage spec, report the above figure with a cursor added to the selected design point:**


- **L vs Vstar:**

 

- **W vs Vstar:**

 

- **Area vs Vstar:**

 


- Calculate the min and max CM input levels. Is the previously selected CM input level in the valid range:

Minimum: $V_{CMmin} = -|V_{GS4}| + |V_{Dsat4}| + 0.6 = -0.2184V$.


Maximum: $V_{CMmax} = -|V_{GS4}| - V_{comp} + V_{DD} = 0.66V$.

Part 2: Differential Amplifier Simulation:

- Differential Amplifier symbol:

 

- Testbench Schematic:

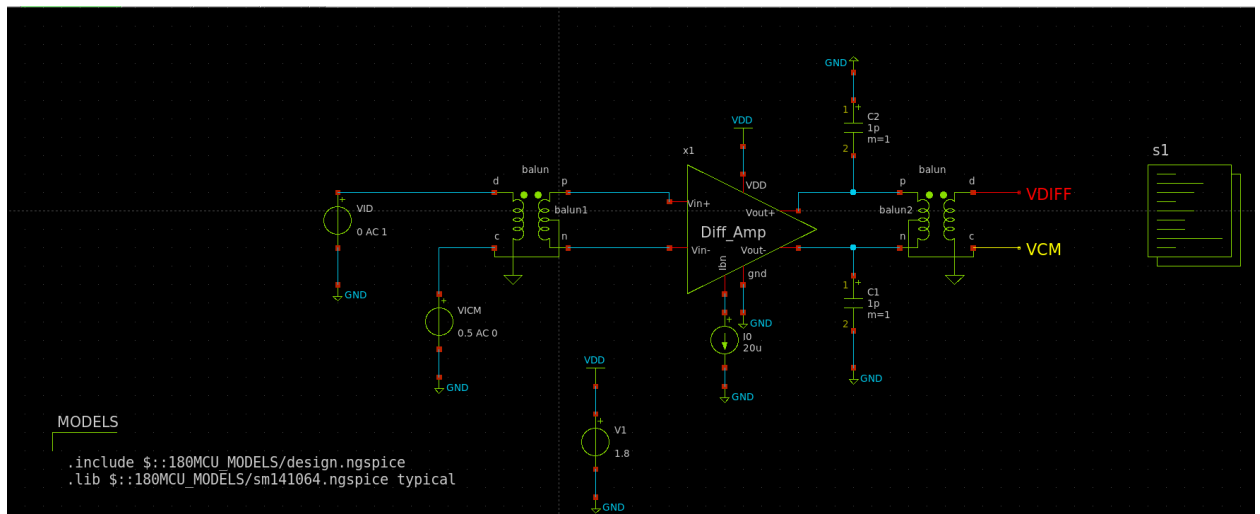

1) OP simulation:

- Report a snapshot clearly showing the following parameters:

device	m.x1.xm4.m0	m.x1.xm3.m0	m.x1.xm2.m0
model	pmos_3p3.12	pmos_3p3.12	pmos_3p3.13
id	1.90478e-05	1.90478e-05	2e-05
gm	0.000281025	0.000281025	0.000205292
gds	3.05838e-06	3.05838e-06	1.01521e-06
vgs	0.938679	0.938679	0.939579
vth	0.874456	0.874456	0.788987
vds	0.927244	0.927244	0.939578
vdsat	0.117562	0.117562	0.166155
gmbs	9.13729e-05	9.13729e-05	9.19137e-05


BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x1.xm1.m0		
model	pmos_3p3.13		
id	3.80956e-05		
gm	0.000390035		
gds	5.79813e-06		
vgs	0.939579		
vth	0.78946		
vds	0.301318		
vdsat	0.165804		
gmbs	0.000174742		

The region can be determined by comparing VDS with VDSat and we find all transistors are in saturation as $VDS > VDSat$. There is no direct way to calculate region in xschem.


2) Diff small signal ccs:

Report the Bode plot of small signal diff gain:

Magnitude in dB:

 

Phase:

 

Gain and BW results:

```
No. of Data Rows : 101
gain                = 7.722126e+00 at= 1.000000e+00
bw                  = 5.673868e+06
binary raw file "lab6_ac.raw"
ngspice 1 ->
```

Hand Analysis:

$$A = gm(RD//ro) = 7.72$$


$$BW = \frac{1}{Cl*(RD//ro)} \text{ then } BW = \frac{1}{27.48*10^3*10^{-12}} = 5.79MHz$$

	Analytical	Simulation
Gain	7.72	7.72
BW	5.79MHz	5.67MHz


3) CM small signal ccs:

Report the Bode plot of small signal CM gain:

Magnitude in dB:

 

Phase:

 

Hand Analysis:

$$ACM = \frac{gm \cdot RD}{1 + gm \cdot 2r_{o1}} = 0.086$$

```
No. of Data Rows : 101
cmgain           = 6.455234e-02 at= 1.000000e+00
binary raw file "lab6_ac.raw"
ngspice 1 -> 
```


	Analytical	Simulation
Gain	0.086	0.06455

Gain is smaller than 1 as in CM the transistor is degenerated with a large resistance r_o of device M1.

Justify the variation of A_{vcm} vs frequency:

At high frequencies the impedance of the capacitance C_L decreases a lot which decreases Z_D and decreases the gain.

 Plot A_{vd}/A_{vcm} in dB. Compare A_{vd}/A_{vcm} @ DC with hand analysis in a table:



Hand Analysis:

$$\frac{A_{vd}}{A_{vcm}} = \frac{7.72}{0.086} = 89.767 = 39dB$$


	Analytical	Simulation
CMRR	39dB	41.56dB

CMRR decreases at high frequencies as CMRR is proportional to R_{SS} and at high frequencies the capacitance associated with the drain of M1 decreases the equivalent impedance.



4) Diff large signal ccs:

Report diff large signal ccs (VODIFF vs VIDIFF). Compare the extreme values with hand analysis in a table.

VODIFF vs VIDIFF:

 

Extreme values:

  

Hand analysis:


At $V_{id} = V_{DD}$: $V_{od} = I_{SS} * R_D = 1.2V$

At $V_{id} = -V_{DD}$: $V_{od} = -I_{SS} * R_D = -1.2V$


	Analytical	Simulation
Vod at Vid=VDD	1.2	1.175
Vod at Vid=-VDD	-1.2	-1.175

 5) CM large signal ccs (GBW vs Vicm):

Report CM large signal ccs (GBW vs VICM):



Common mode input range:

 

Hand analysis was done in first part.

	Analytical	Simulation
VICM min	-0.2184	−0.43
VICM max	0.66	0.81