 


Lab 07


Part 1: gm/ID Design Charts:

Using ADT Device Xplore, plot the following design charts vs gm/ID for both PMOS and NMOS.
Set $V_{DS} = V_{DD}/3$ and $L = 0.28\mu, 0.4\mu:0.4\mu:2\mu$:


- NMOS:
 - gm/gds




- ID/W

 

- gm/cgg

 


- VGS

 


- PMOS:


- gm/gds

 


○ ID/W

 

○ gm/cgg

 

○ VGS

 

Part 2: OTA Design:

- **Specs:**

Parameter	value
VDD	1.8V
Load	5pF
Open loop dc voltage gain	$\geq 34 \text{ dB}$
CMMR at dc	$\geq 74 \text{ dB}$
Phase margin	$\geq 70^\circ$
CM input range low	$\leq 1 \text{ V}$
CM input range high	$\geq 1.5 \text{ V}$
GBW	$\geq 10 \text{ MHz}$

- **Detailed design procedure and hand analysis:**

- We will choose a single stage 5T-OTA as the gain isn't very high and we can use a single stage to achieve it. The input pair will be NMOS as the CM input range is closer to VDD.
- First, we will design the input pair. We know that $GBW = \frac{gm_{12}}{2\pi * CL} \geq 10 \text{ MHz}$ then $gm_{12} \geq 314.16 \mu S$. Taking margin, we will choose $gm = 320 \mu S$.
- We will assume a reasonable gm/ID value 16 so the current in each branch will be $20 \mu A$.
- We will assume that $ro_{12} = ro_{34}$ then from the gain spec we want $\frac{gm}{2 * gds} \geq 50$ then $gds \leq 3.1416 \mu S$, we will take a margin and choose $gds = 3 \mu S$.
- There is a body effect in the input pair we will assume approximate value of 0.35V and put $V_{DS} = 0.6 \text{ V}$ as given.
- From the SA values in the next page, we $W = 17.29 \mu m$ and $L = 450 \text{ nm}$.

Plot 1APlot 1BPlot 1CPlot 1D

Import: Plot 1DOK?

LUT Settings

ID20u?

gm/ID16?

gds3u?

VDS0.6?

VSB0.35?

Stack1?

Results:

	Name	TT-27.0
1	ID	20u
2	IG	N/A
3	L	450n
4	W	17.29u
5	VGS	838.3m
6	VDS	600m
7	VSB	350m
8	gm/ID	15.65
9	Vstar	127.8m

Y-Expr gm/cgg?

Plot

Plot 1APlot 1BPlot 1CPlot 1D

Import: Plot 1DOK?

LUT Settings

ID20u?

gm/ID16?

gds3u?

VDS0.6?

VSB0.35?

Stack1?

Results:

	Name	TT-27.0
10	ft	2.262G
11	gm/gds	107.6
12	VA	6.876
13	ID/W	1.157
14	gm/W	18.1
15	AREA	7.781p
16	gm	313u
17	gmb	88.1u
18	gds	2.909u

Y-Expr gm/cgg?

Plot

Plot 1APlot 1BPlot 1CPlot 1D

Import: Plot 1DOK?

LUT Settings

ID20u?

gm/ID16?

gds3u?

VDS0.6?

VSB0.35?

Stack1?

Results:

	Name	TT-27.0
19	ro	343.8k
20	Ron	30k
21	VTH	810.1m
22	VDSAT	102.9m
23	cgg	22.02f
24	cdd	12.15f
25	csg	9.87f
26	cdg	7.658f
27	cgd	3.265f

Y-Expr gm/cgg?

Plot

- Now, we will design the active load transistors. We know that $ID = 20\mu A$ in each branch from the input pair design. We also assumed that $gds_{12} = gds_{34} = 3\mu S$.
- From CM input range high $V_{CM} = V_{th1,2} - |V_{GS3,4}| + V_{DD} \geq 1.5$
We got $V_{GS1,2} \approx 0.84V$ and $V_{Dsat1,2} \approx 0.1$ then $V_{GS3,4} \leq 1.11$
We got $W = 2.81\mu m$ and $L = 340nm$.

Plot 1APlot 1BPlot 1CPlot 1D

Import: Plot 1DOK?

LUT Settings

ID20u?

VGS1.1?

gds3u?

VDS0.6?

VSB0?

Stack1?

Results:

	Name	TT-27.0
1	ID	19.75u
2	IG	N/A
3	L	340n
4	W	2.81u
5	VGS	1.1
6	VDS	600m
7	VSB	0
8	gm/ID	5.064
9	Vstar	395m

Y-Expr gm/cgg?

Plot

Plot 1APlot 1BPlot 1CPlot 1D

Import: Plot 1DOK?

LUT Settings

ID20u?

VGS1.1?

gds3u?

VDS0.6?

VSB0?

Stack1?

Results:

	Name	TT-27.0
10	ft	3.878G
11	gm/gds	33.68
12	VA	6.652
13	ID/W	7.03
14	gm/W	35.6
15	AREA	955.4f
16	gm	100u
17	gmb	38.61u
18	gds	2.97u

Y-Expr gm/cgg?

Plot

Plot 1APlot 1BPlot 1CPlot 1D

Import: Plot 1DOK?

LUT Settings

ID20u?

VGS1.1?

gds3u?

VDS0.6?

VSB0?

Stack1?

Results:

	Name	TT-27.0
19	ro	336.7k
20	Ron	30.37k
21	VTH	761.9m
22	VDSAT	327.7m
23	cgg	4.105f
24	cdd	1.852f
25	csg	2.043f
26	cdg	1.527f
27	cgd	461.2a

Y-Expr gm/cgg?

Plot

- Now, we will design the tail current mirror. We know that the current in the transistor is $40\mu A$.
- From the CM input range low: $V_{CM} = V_{GS1,2} + V_{Dsat5} \leq 1$ then $V_{Dsat5} \leq 0.16$.
And we know that v^* is always higher than V_{dsat} then we may choose $v^* = 0.2V$.
From CMRR spec we find that $ACM \leq -40dB$ then $\frac{1}{2 \cdot g_{m3,4} \cdot r_{o5}} \leq 0.01$. $r_{o5} \geq 500K\Omega$.
- We put $V_{DS}=0.35V$ as we put the V_{SB} for the input pair with the same value and $V_{SB1,2} = V_{DS5}$.
- We got $W = 28.23\mu m$ and $L = 1.48\mu m$.
- To get sizing for M6: $L_6=L_5=1.48\mu m$ and $\frac{W_6}{W_5} = \frac{10\mu A}{40\mu A}$ then $W_6 = 7.0575\mu m$.

The image shows three screenshots of a simulation tool's LUT (Look-Up Table) settings and results for three different plots (Plot 1A, Plot 1B, Plot 1C, Plot 1D). Each plot has the same LUT settings: ID=40u, Vstar=0.2, ro=500k, VDS=0.35, VSB=0, Stack=1. The results tables show various parameters for each plot.

Name	TT-27.0
1 ID	40u
2 IG	N/A
3 L	1.48u
4 W	28.23u
5 VGS	825.8m
6 VDS	350m
7 VSB	0
8 gm/ID	10
9 Vstar	200m

Name	TT-27.0
10 fT	515.2MEG
11 gm/gds	199
12 VA	19.89
13 ID/W	1.417
14 gm/W	14.17
15 AREA	41.78p
16 gm	400.1u
17 gmb	155.3u
18 gds	2.011u



Name	TT-27.0
19 ro	497.3k
20 Ron	8.75k
21 VTH	676.3m
22 VDSAT	165.2m
23 cgg	123.6f
24 cdd	23.31f
25 csg	60.78f
26 cdg	42.82f
27 cgd	5.961f

• **Transistors calculated parameters:**

NUM	W	L	gm	ID	gm/ID	VDsat	Vov	V*
M1,2	17.3 μm	450nm	313 μS	20 μA	15.65	103mV	28.2mV	127.8mV
M3,4	2.8 μm	340nm	100 μS	20 μA	5	327.7mV	338.1mV	400mV
M5	28.2 μm	1.48 μm	400 μS	40 μA	10	165.2mV	149.5mV	200mV
M6	7.05 μm	1.48 μm	100 μS	10 μA	10	165.2mV	149.5mV	200mV

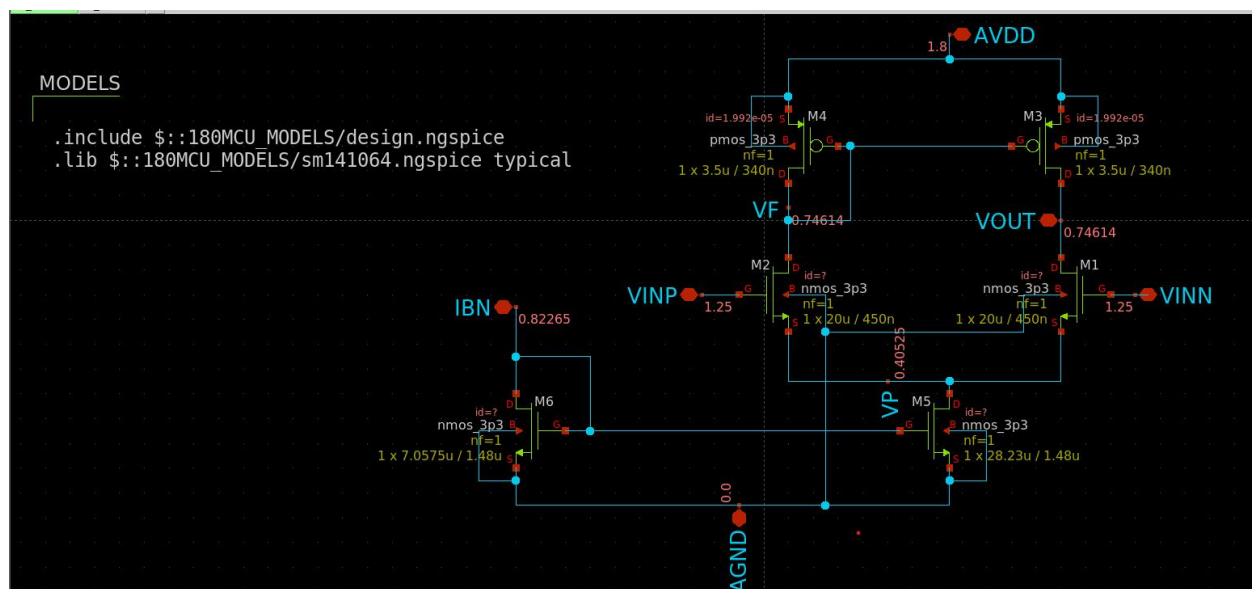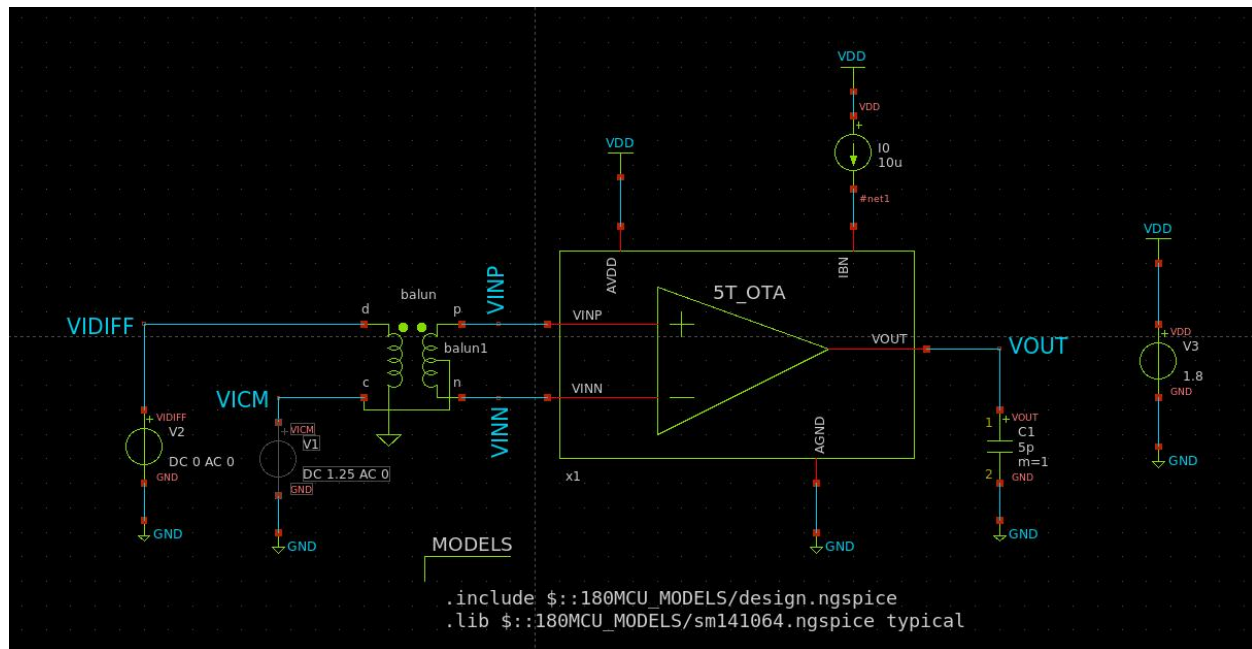Part 3: Open-Loop OTA Simulation:

Schematic of the OTA with DC node voltages clearly annotated:



```

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m.x1.xm6.m0      m.x1.xm4.m0      m.x1.xm3.m0
model       nmos_3p3.10     pmos_3p3.8       pmos_3p3.8
id          1e-05          1.99096e-05      1.99096e-05
gm          0.000101295    0.000102627      0.000102627
gds         2.5173e-07     1.8722e-06       1.8722e-06
gmbs        3.94132e-05    3.96305e-05      3.96305e-05
vgs         0.822648       1.09261          1.09261
vth         0.676836       0.757213         0.757213
vds         0.822646       1.0926           1.0926
vdsat       0.163568       0.326462         0.326462
cgs         -2.27501e-14         -2.51545e-15     -2.51545e-15
cgd         -4.94816e-18       9.29301e-18      9.29301e-18
csb         -5.54631e-15         -6.02479e-16     -6.02479e-16
cdb         -3.70319e-15         -4.02314e-16     -4.02314e-16

```

```

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m.x1.xm5.m0      m.x1.xm2.m0      m.x1.xm1.m0
model       nmos_3p3.14     nmos_3p3.12      nmos_3p3.12
id          3.98192e-05     1.99096e-05      1.99096e-05
gm          0.000404564     0.00031354       0.00031354
gds         1.59919e-06     4.21413e-06      4.21413e-06
gmbs        0.000157466     8.61308e-05      8.61308e-05
vgs         0.822648       0.852176         0.852176
vth         0.677106       0.826178         0.826178
vds         0.397819       0.309558         0.309558
vdsat       0.1638         0.102298         0.102298
cgs         -9.11125e-14         -9.5649e-15      -9.5649e-15
cgd         -2.22179e-16         -4.03201e-18     -4.03201e-18
csb         -2.22359e-14         -1.68521e-15     -1.68521e-15
cdb         -1.49567e-14         -1.13408e-15     -1.13408e-15

```

```

=== Calculated Parameters ===
M1: gm/id = 15.7481 S/A, Vstar = 0.126999 V, ro = 237297 ohms
M2: gm/id = 15.7481 S/A, Vstar = 0.126999 V, ro = 237297 ohms
M3: gm/id = 5.15467 S/A, Vstar = 0.387998 V, ro = 534132 ohms
M4: gm/id = 5.15467 S/A, Vstar = 0.387998 V, ro = 534132 ohms
M5: gm/id = 10.16 S/A, Vstar = 0.19685 V, ro = 625316 ohms
M6: gm/id = 10.1295 S/A, Vstar = 0.197443 V, ro = 3.97251E+06 ohms
ngspice 1 -> █

```

The change in $ro_{1,2}$ and $ro_{3,4}$ is because of the change in VDS

Note: I changed $W_{1,2}$ and $W_{3,4}$ slightly as some specs weren't achieved. We will discuss this at its part and the updated OP will be in the updated section.

- Is the current (and gm) in the input pair exactly equal?


Yes, the current and gm of the input pair is equal as they have the same bias point and no mismatch.

- What is DC voltage at VOUT? Why?


$V_{out} = 0.746V$ as it can be got from $v_{out} = VF = VDD - |V_{GS3,4}| = 0.746$ and $V_{out}=VF$ as if we tried to assume $V_{out}<VF$ then $V_{DS3}>V_{DS4}$ and M_3,M_4 have the same VGS which means more current in the right branch but $V_{DS1}<V_{DS2}$ which means more current in the left branch so it is wrong and if we assumed $V_{out}>VF$ we will get the same result so $V_{out}=VF$.

2) Diff small signal ccs:

- Diff gain in dB:

 

- Diff gain phase:

 


- Hand Analysis:
 $Ad = gm_{1,2} * (ro_{1,2} // ro_{3,4}) = 51.5 = 34.24dB.$


	Hand Analysis	Simulation
Diff gain	34.24dB	34.16dB

3) CM small signal ccs:

- CM gain in dB:

 

- CM gain phase:

 

Note: the phase here is calculated from -180 to 180 but if it was calculated from 0 to 360 the graph would be smooth without this sharp transition.

The increase of CM gain at high frequencies is because at high frequencies the capacitors at node VP will have low impedance which reduces the degeneration impedance and increases the CM gain.


- Hand Analysis:

$$ACM = \frac{1}{2 * gm_{3,4} * r_{o5}} = 7.79 * 10^{-3} = -42.16dB$$

	Hand Analysis	Simulation
CM gain	$-42.16dB$	$-44.54dB$

4) CMRR:

- Plot VOUT vs VID:

 

- Hand Analysis:

$$CMRR = \frac{A_d}{A_{CM}} = 6611 = 76.4dB.$$


	Hand Analysis	Simulation
CMRR	$76.4dB$	$78.7dB$

 5) Diff large signal ccs:

- Plot VOUT vs VID:




- From the plot, what is the value of V_{out} at $VID = 0$? Why?



$V_{out} = 0.7073$ approximately equals what we got when we got at page 7 V_{out} was 0.746 and this is expected as at $VID=0$ this is CM Bias so they should be the same and equal V_F .

 
- Plot the derivative of V_{OUT} vs V_{ID} . Compare the peak with A_{vd} :



The peak = 60.55 and $A_{vd} = 51$ so the peak is higher than A_{vd} but they should be the same value as they are the same thing but may be the problem is that the slope is very high so any small change changes the value and the step is quite high which increases the error in calculating the slope.

6) CM large signal ccs (GBW vs VICM):

- Plot GBW vs VICM:

 


- Annotate the CM input range. Calculate the input range as the range over which the GBW is within 90% of the max GBW, i.e., 10% reduction in GBW

```

No. of Data Rows : 101
gain              = 1.373074e-01 at= 1.000000e+00
bw               = 5.853156e+06
max_gbw          = 1.010622e+07 at= 7.943282e+05
min_vincm        = 8.633484e-01
max_vincm        = 1.510460e+00
min_vincm = 8.633484e-01
max_vincm = 1.510460e+00
cmir = 6.471116e-01
binary raw file "5t_ota_tb_cmir1.raw"


```

 


- We have $0.8633 < V_{ICM} < 1.51$ and the input range = $0.647V$.
- The V_{ICM} max and GBW specs weren't achieved so
- First, We changed $W_{3,4}$ from $2.8\mu m$ to $3.5\mu m$ to decrease $V_{star3,4}$ so decrease $V_{GS3,4}$ and we know $V_{CMmax} = V_{th1,2} - |V_{GS3,4}| + V_{DD}$ so we achieved the V_{CM} max spec.
- Second, We changed W from $17.3\mu m$ to $20\mu m$ to increase $g_{m1,2}$ for the same current so increase the GBW.

Checking that all specs are achieved after the edit of values:

Open loop DC gain:

 

CMRR:

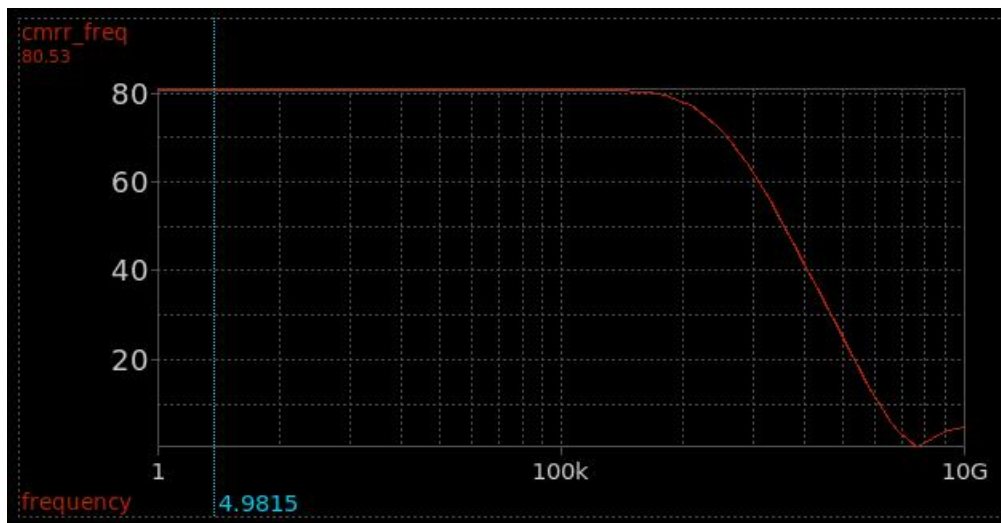

- And the specs on GBW and CM input range are achieved in the last section so all specs are achieved.


OP after edit:

BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x1.xm6.m0	m.x1.xm4.m0	m.x1.xm3.m0
model	nmos_3p3.10	pmos_3p3.8	pmos_3p3.8
id	1e-05	1.99155e-05	1.99155e-05
gm	0.000101295	0.000116359	0.000116359
gds	2.5173e-07	1.97368e-06	1.97368e-06
gmbs	3.94132e-05	4.48433e-05	4.48433e-05
vgs	0.822648	1.05386	1.05386
vth	0.676836	0.759278	0.759278
vds	0.822646	1.05385	1.05385
vdsat	0.163568	0.292858	0.292858
cgs	-2.27501e-14	-3.10674e-15	-3.10674e-15
cgd	-4.94816e-18	1.15095e-17	1.15095e-17
csb	-5.54631e-15	-7.46806e-16	-7.46806e-16
cdb	-3.70318e-15	-4.98697e-16	-4.98697e-16

BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x1.xm5.m0	m.x1.xm2.m0	m.x1.xm1.m0
model	nmos_3p3.14	nmos_3p3.12	nmos_3p3.12
id	3.98309e-05	1.99155e-05	1.99155e-05
gm	0.000404684	0.000325502	0.000325502
gds	1.56692e-06	3.93367e-06	3.93367e-06
gmbs	0.000157513	8.90995e-05	8.90995e-05
vgs	0.822648	0.844747	0.844747
vth	0.677106	0.8281	0.8281
vds	0.405248	0.340883	0.340883
vdsat	0.1638	0.0973635	0.0973635
cgs	-9.11035e-14	-1.04883e-14	-1.04883e-14
cgd	-2.08558e-16	3.48632e-18	3.48632e-18
csb	-2.22338e-14	-1.84823e-15	-1.84823e-15
cdb	-1.49491e-14	-1.24124e-15	-1.24124e-15

PART 4: Closed-Loop OTA Simulation:

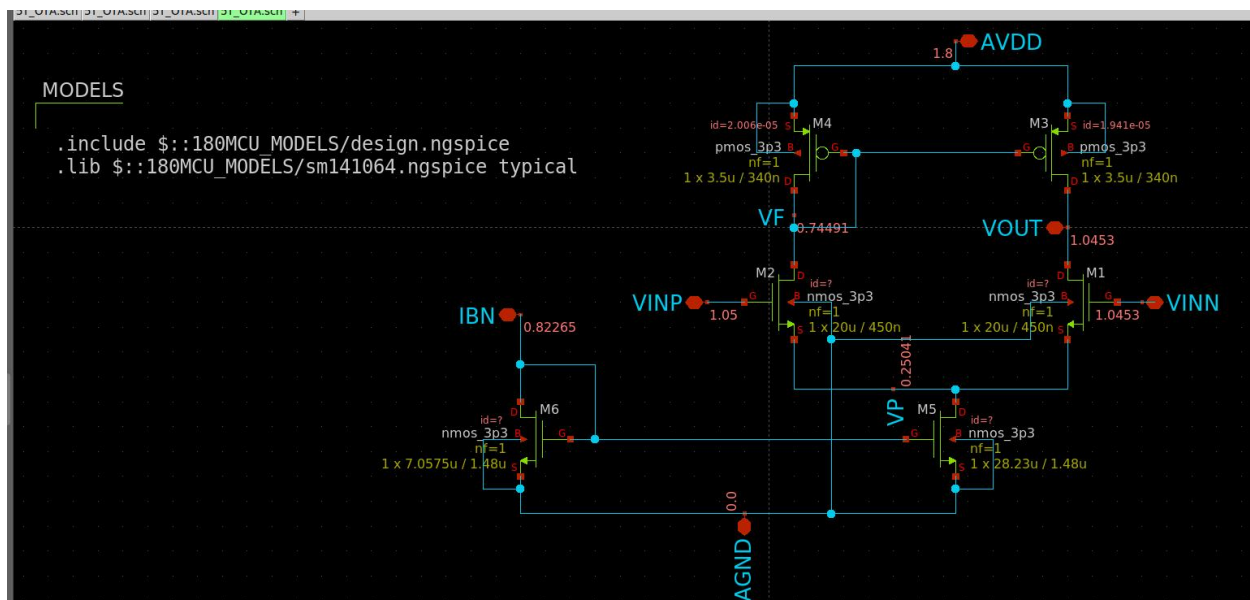1) Schematic of the OTA with DC OP point clearly annotated:



```

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m.x1.xm6.m0      m.x1.xm4.m0      m.x1.xm3.m0
model       nmos_3p3.10      pmos_3p3.8       pmos_3p3.8
id          1e-05            2.00605e-05      1.94124e-05
gm          0.000101295      0.000116741      0.000113419
gds         2.5173e-07       1.98442e-06      2.37575e-06
gmbs        3.94132e-05      4.49942e-05      4.38298e-05
vgs         0.822648         1.05508          1.05508
vth         0.676836         0.759271         0.760992
vds         0.822646         1.05507          0.754642
vdsat       0.163568        0.293854         0.292466
cgs         -2.27501e-14     -3.10768e-15     -3.11105e-15
cgd         -4.94816e-18     1.15122e-17      8.45108e-18
csb         -5.54631e-15     -7.46937e-16     -7.49228e-16
cdb         -3.70318e-15     -4.98784e-16     -5.01718e-16


```

```

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m.x1.xm5.m0      m.x1.xm2.m0      m.x1.xm1.m0
model       nmos_3p3.14      nmos_3p3.12      nmos_3p3.12
id          3.94729e-05      2.00605e-05      1.94124e-05
gm          0.000399697      0.000328428      0.000320694
gds         4.12506e-06      3.18934e-06      2.65419e-06
gmbs        0.000155591      9.67358e-05      9.44281e-05
vgs         0.822648         0.799593         0.794937
vth         0.677106         0.784446         0.783693
vds         0.250403         0.494505         0.794935
vdsat       0.1638          0.096036         0.0940614
cgs         -9.14452e-14     -1.03867e-14     -1.014e-14
cgd         -1.11189e-15     1.43793e-17      1.85473e-17
csb         -2.23542e-14     -1.98344e-15     -1.93907e-15
cdb         -1.53579e-14     -1.32668e-15     -1.29428e-15

```

- Closed loop schematic:

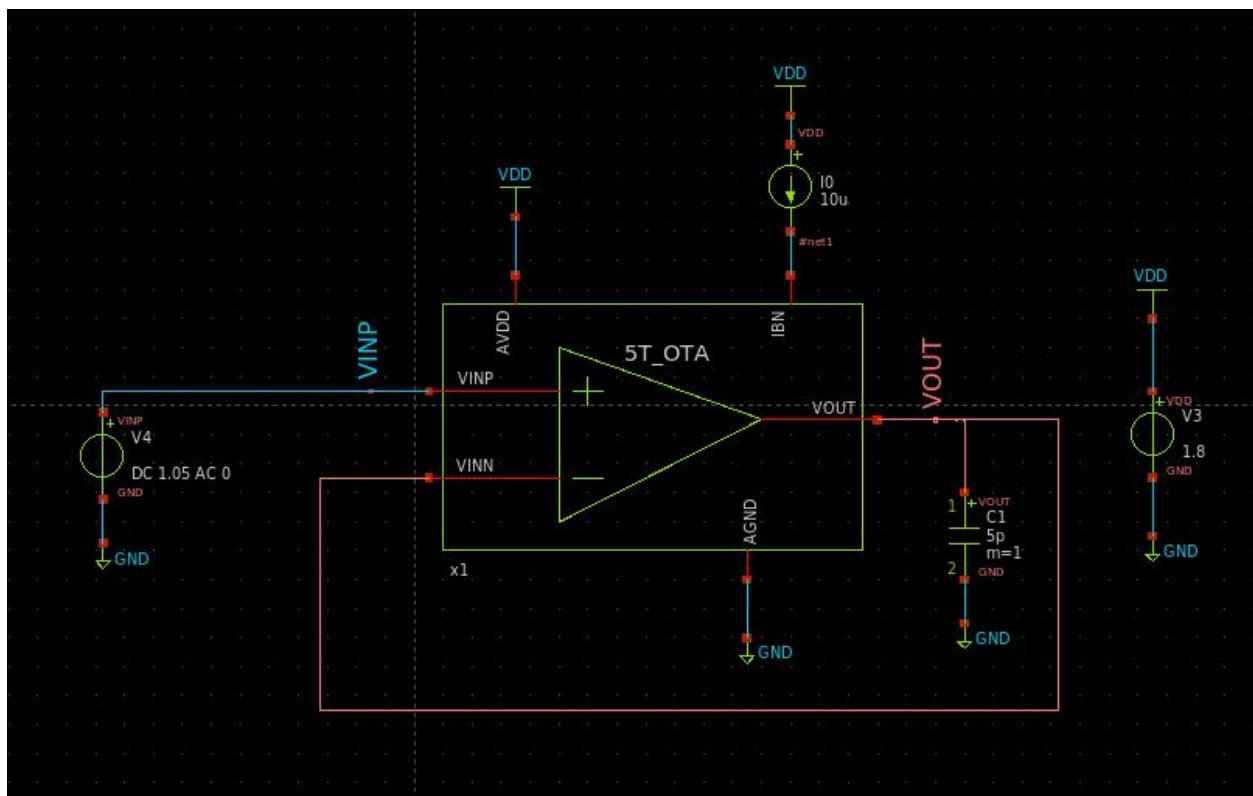

- Is the current (and gm) in the input pair exactly equal? Why?

No, they aren't equal as $AOL = \frac{V_{out}}{V_{err}}$ _and note that Vout here is the change in Vout_ from this relation we find that Verr has a small value we can calculate it $V_{err} = \frac{1.05 - 0.746}{51.5} = 5.9 * 10^{-3}$ and we know that $V_{err} = V_{INP} - V_{INN} = 1.05 - V_{INN} = 5.9 * 10^{-3}$ then $V_{INN} = 1.044$. ad this change in VGS changes the current and gm more current will be in the branch of VINP as it has higher VGS.


- Calculate the mismatch in ID and gm:

$$\text{Current mismatch} = \frac{20 - 19.4}{20} * 100 = 3\%$$


$$\text{gm mismatch} = \frac{328.4 - 320.7}{328.4} * 100 = 2.3447\%$$

 2) Loop gain:

- Plot loop gain in dB and phase vs frequency:



- LG phase:

 

- PM spec:

```
gain_crossover_freq = 9.565370e+06
phaseatzerogain     = 9.042466e+01
pm = 8.957534e+01
```

➤ We can find that $PM = 89.5 > 70$ which meets the spec.

- **Compare DC gain and GBW with those obtained from open-loop simulation. Comment.**

	Loop gain	Open loop
Gain	54	54.64
GBW	9.565MHz	10MHz

- Comment:

The $LG = \beta * A_{ol}$ and $\beta=1$ then $LG = A_{ol}$ and it is expected to have the same gain and GBW. We took GBW for LG =gain cross over freq but it will be slightly higher.

Closed loop results:

```
gain          = 9.791690e-01 at= 1.000000e+00
bw            = 1.007271e+07
gbw = 9.862885e+06
binary raw file "Lab7_AC.raw"
```

	Closed loop	Open loop
Gain	0.979	54.64
GBW	9.86MHz	10MHz

- Comment:

➤ The closed loop gain is divided by the factor $(1+LG)$ which equals 55.64 so

$ACL = \frac{54.64}{55.64} = 0.982$ which is true and GBW was expected to be the same as the BW will increase with the same factor $(1+LG)$ so GBW is constant which is approximately true.

- **Compare simulation results with hand calculations in a table:**

Hand Analysis:

$$ACL = \frac{54.64}{55.64} = 0.982 .$$

$$GBW_{cl} = GBW_{ol} = 10MHz.$$

	Hand Analysis	Simulation
Gain	0.982	0.979
GBW	10MHz	9.86MHz

Spec comparison:

Parameter	required	result
Open loop dc voltage gain	$\geq 34 \text{ dB}$	34.75dB
CMMR at dc	$\geq 74 \text{ dB}$	78.7dB
Phase margin	$\geq 70^\circ$	89.5°
CM input range low	$\leq 1 \text{ V}$	0.8633V
CM input range high	$\geq 1.5 \text{ V}$	1.51V
GBW	$\geq 10 \text{ MHz}$	10MHz